
## Ex 12

Implementation of Higher order MUX using Lower order.

Nihal Shah Parekkattil RA1911003010868


- ❖ AIM : To implement :
  - 1. 8:1 using 4:1
  - 2. 16:1 using 8:1
  - 3. 16:1 using 4:1

## • Implementation of 8:1 using 4:1

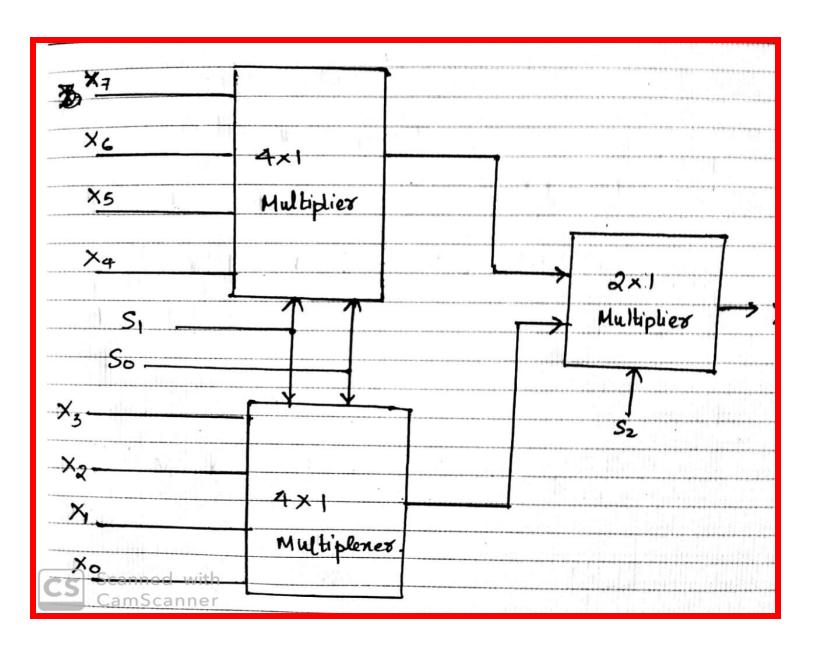

Truth table						
·	11.11	Output				
Sa	Sı	So	Y			
		•				
O	0	0	Xo			
0	0	on still	× , , , , ,			
0	1	10	Xe			
10	5/11	11 1 1	X3			
	0	<b>O</b> .F.	X4			
	0		X5			
	1	0	Xé			
1	1	)	X2 X3 X4 X5 X6 X4			
CS Scanned CamSca	with	V.				


**Truth table of 8\*1 MUX** 

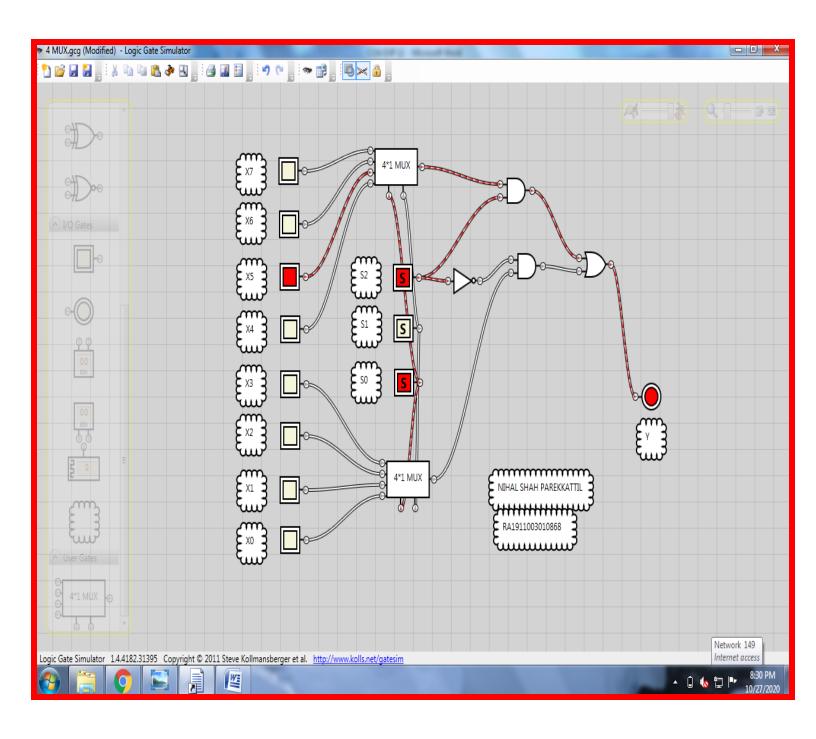


· · · · · · · · · · · · · · · · · · ·							
		Output					
\$3	S,	S.	So	У			
				*,			
0	0	0	0	1- 1 X0 12.			
O	0	0	1	×,			
0	0	4	0	× <sub>2</sub>			
000	0	- 1	1	X3 01110			
0	i	0	0	Хц			
0	1	0	1	X5 101			
0		1	0	Xe			
O	1111	3	1	X			
rapail	0	0	0	, X8			
1		0	1	Xq1/- X10			
1	D	1	0	× to			
10	) )0	<b>J</b> ,	1 1	100,100			
11	,	0	0	X <sub>12</sub>			
		0	1	X13			
1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	1 1	111111	0	X <sub>12</sub> X <sub>13</sub> X <sub>14</sub> X <sub>15</sub>			
1	100	1	131 1	X 15			
CS Scar	nred with						

**Truth table of 16\*1 MUX** 

## • Implementation of 16:1 using 8:1

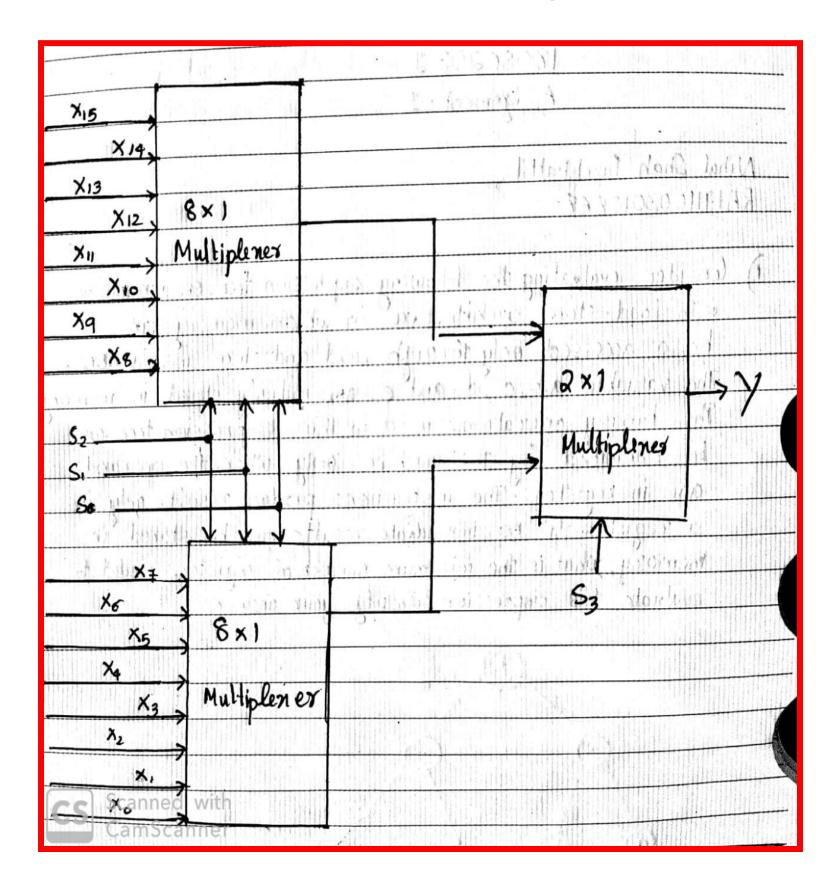

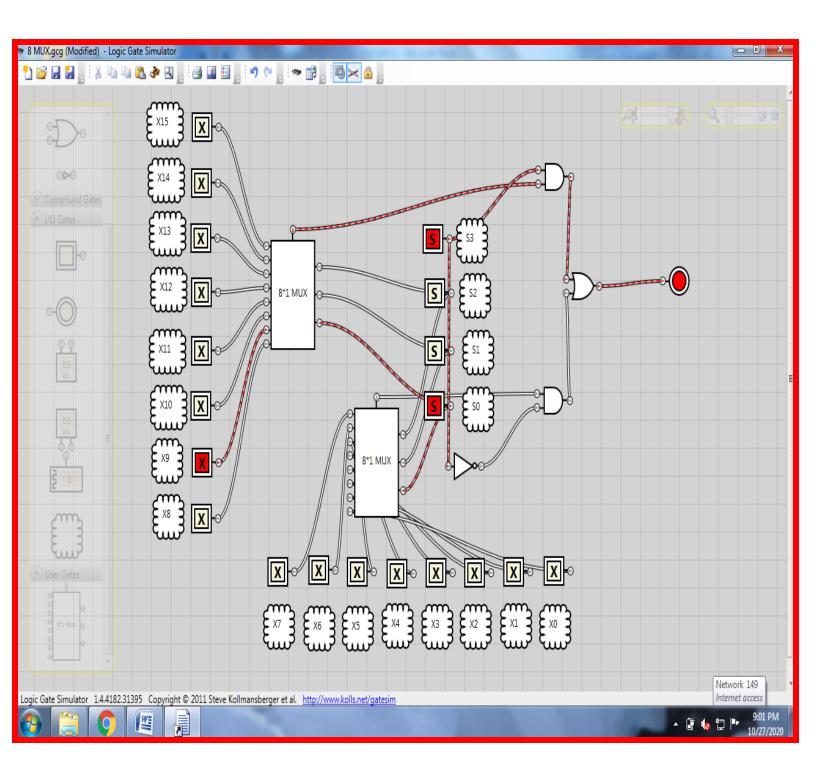

## • Implementation of 16:1 using 4:1

